

Electricity Basics

Electricity basics


The flow of electrical current through a wire is a flow of electrons.

It is analogous to the *flow of water through a pipe*

Voltage is similar to *water pressure*. It is **noted V** and **measured in Volts**

Current is similar to *flow rate*. It is **noted I** and **measured in Amperes**

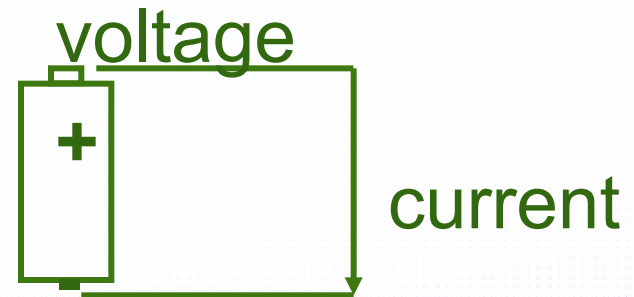For a same wire (/pipe),
the higher the voltage (/pressure),
the higher the current (/flow rate)



Resistance

- Resistance is the opposition to the passage of an electric current
 - Symbol: '**R**' (resistance)
 - Unit: '**Ω**' (Ohms)
- The smaller the pipe, the greater the resistance to water flow
- The thinner the wire, the greater the resistance to electric current
- A traditional incandescent light bulb is a high resistance wire

Key Formula 1: Ohm's Law

- Current, Voltage and Resistance are related.
If you know any two you can calculate the third

$$V = I \times R$$

$$2 \text{ A} \times 0.1 \text{ } \Omega = 0.2 \text{ V}$$

$$20 \text{ A} \times 0.1 \text{ } \Omega = 2.0 \text{ V}$$

$$R = V / I$$

$$12\text{V} / 1.0 \text{ A} = 12.0 \text{ } \Omega$$

$$I = V / R$$

$$12\text{V} / 2.0 \text{ } \Omega = 6.0 \text{ A}$$

$$110\text{V} / 2.0 \text{ } \Omega = 55 \text{ A}$$

What happens if you plug into 110V a bulb designed for 12V?

Power & Energy



- Power is measured in W (Watt) and it is the rate at which energy is generated or consumed at a given time
- Energy is measured over time in Wh (Watt-hour). That's what the electricity company usually bills for.
- When a 1 W appliance is used for one hour, the energy used is 1 Wh
- Energy can be stored in a battery, like water stored in a bucket or pond

Power & Energy Examples

- If power rating of an incandescent light bulb is 60 Watts (W)

and the bulb is used for 5 hours a day

Its total energy used per day is
 $60 \text{ W} * 5 \text{ hours} = 300 \text{ Watt-hours (Wh)}$



- If power consumption for a color TV is 100 Watts (W) and it is used for 2 hours a day

Its total energy use per day is
 $100 \text{ W} \times 2 \text{ hours} = 200 \text{ Wh}$



Key Formula 2: Electrical Power

The power used by an electrical device is calculated as:

Power = Voltage x Current


$$P = V \times I$$

Examples: 60 Watts = 12 Volts x 5 Amp

60 Watts = 120 Volts x .5 Amp

DC vs. AC

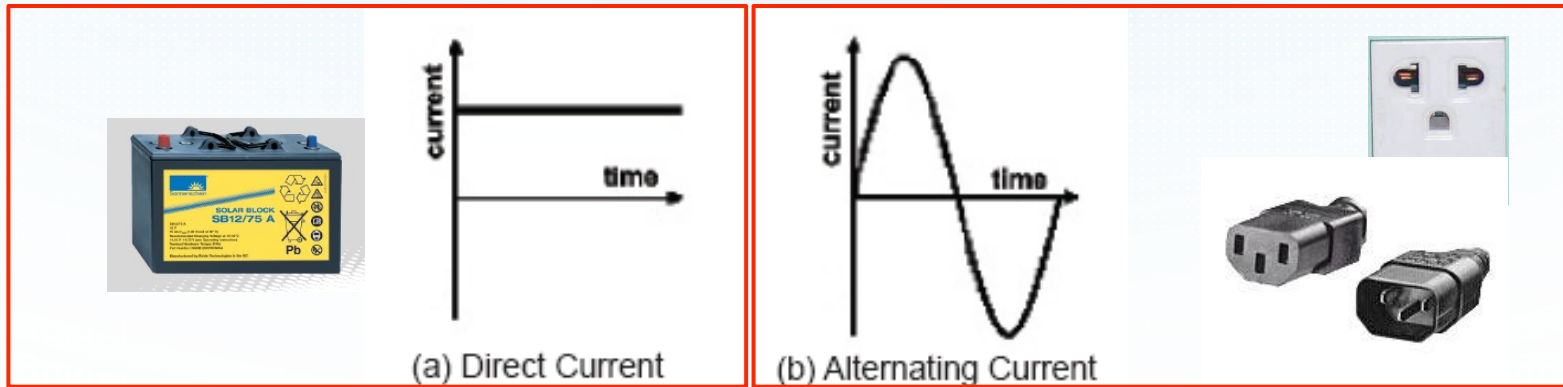Electricity from a battery or solar panel is called Direct Current (DC)
There is a Positive contact/wire (+) and a Negative (-)



The grid electricity is Alternative Current (AC)



Each wire changes from + to – 50 times or 60 times per second

Devices made for one type of current CANNOT be used with the other
When measuring V or I, need to use different multimeter settings

AC Advantages

- The main advantage of AC over DC is that transformers can be used to change the AC voltage from a lower value to the higher value or the other way around
 - That is 230 Volts AC can be easily raised to 1000 Volts AC, or 230 Volts AC can be lowered to 110 Volts or 12V AC
- Another advantage is that it can run AC motors that are simpler in construction than the equivalent DC motors

Simple electrical circuit

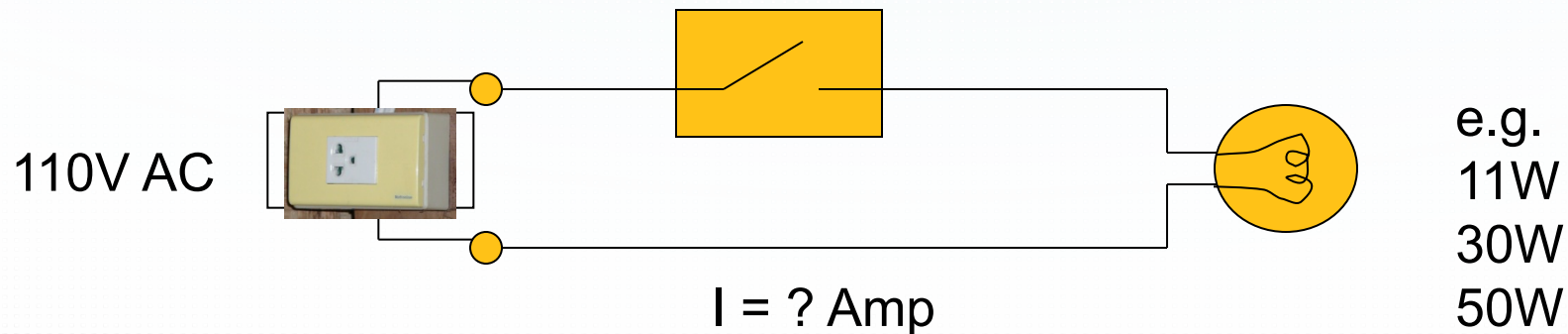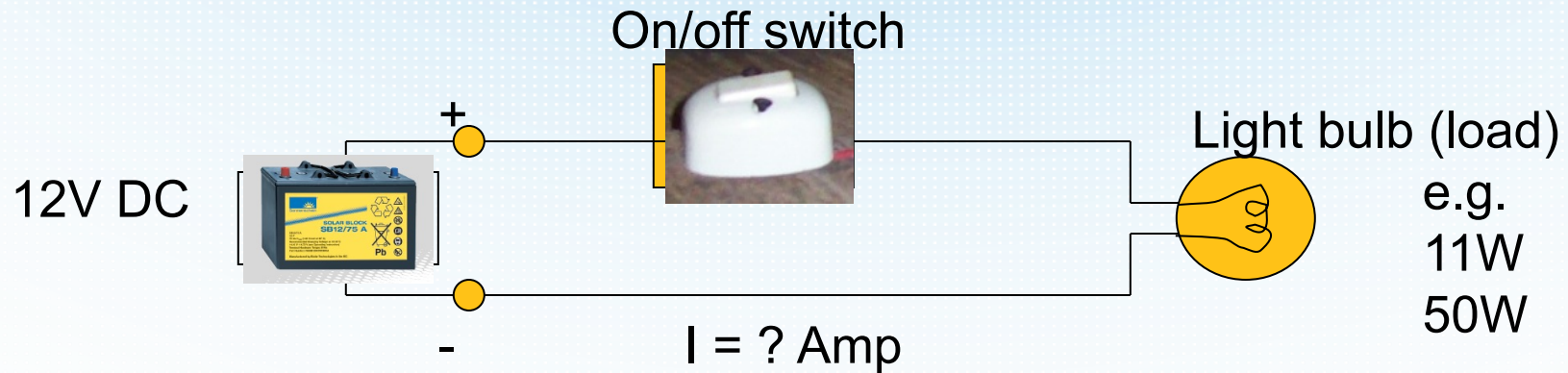


Remember: $P = V \times I$


$I = P / V$

Series vs. parallel

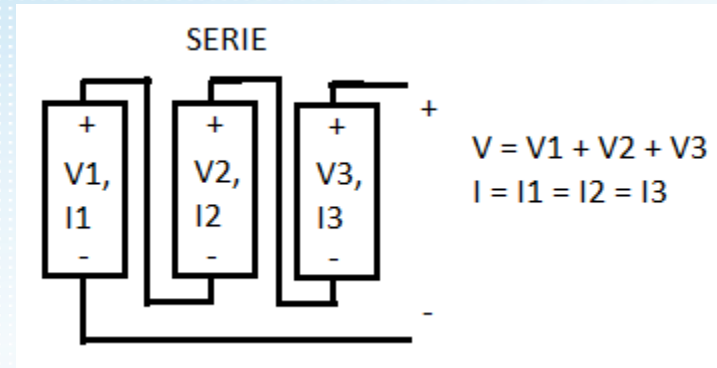
- When devices are connected in **series**,
- The same current passes through all components: $I = I_1 = I_2$ etc.
 - In DC the (+) contact of one device is connected to the (-) of the next one.
 - The voltage across the full circuit is the sum of the voltages across all components.
 $V = V_1 + V_2 + V_3$, etc.



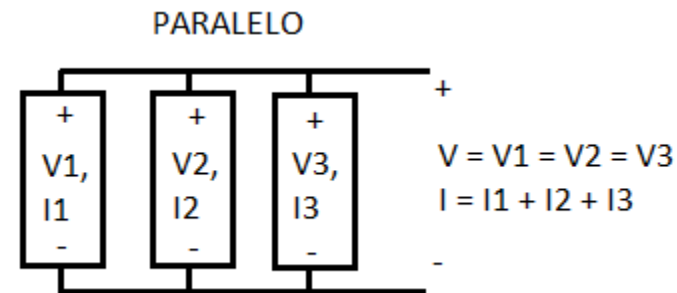
- When components are connected in **parallel**, the current is split between all
- In DC, the contacts of same polarity (+) or (-) are connected together
 - The voltage is the same across all components: $V = V_1 = V_2 = V_3$,
 - The total current is the sum of currents in each branch: $I = I_1 + I_2 + I_3$.



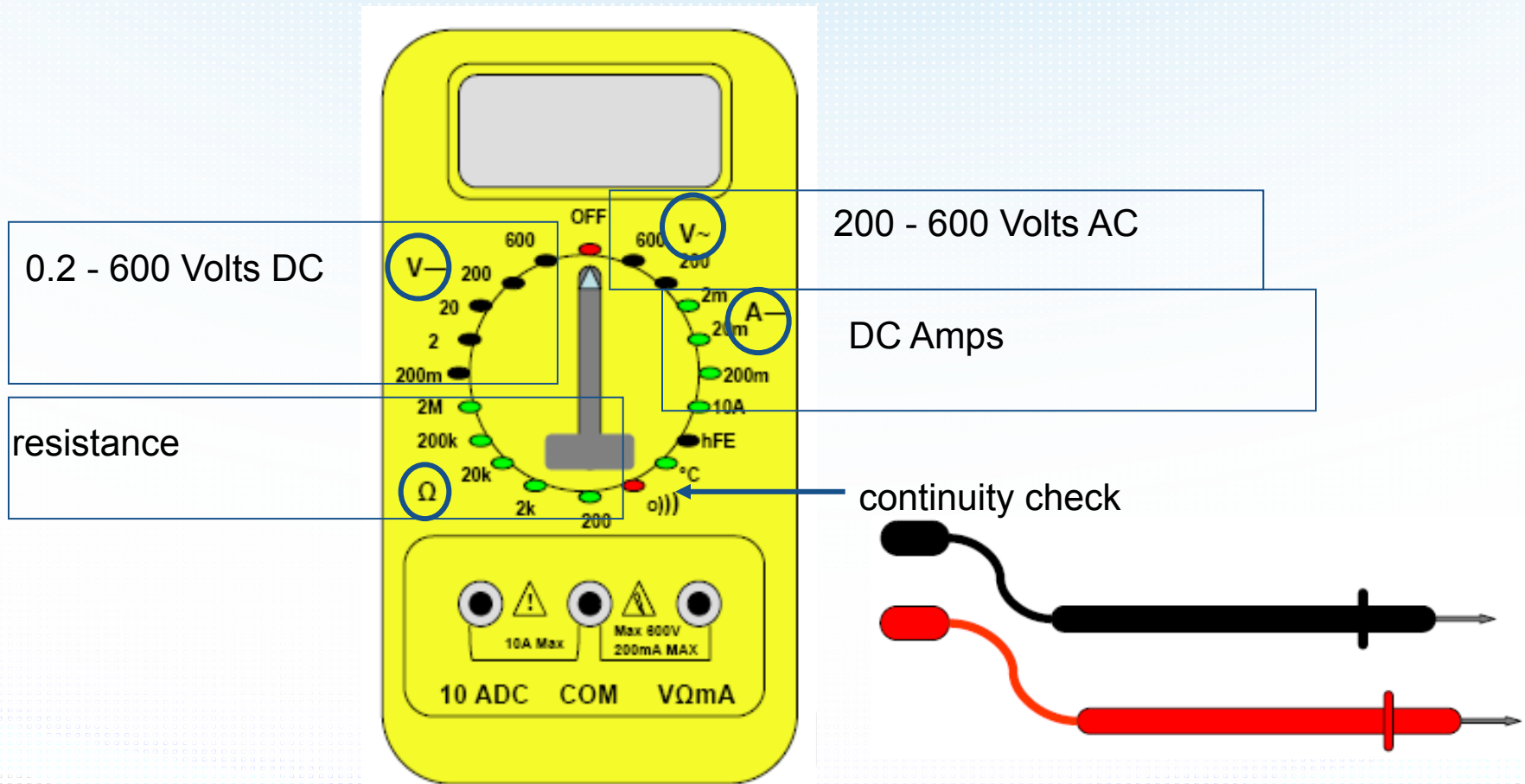Using a Voltmeter: select what will be measured




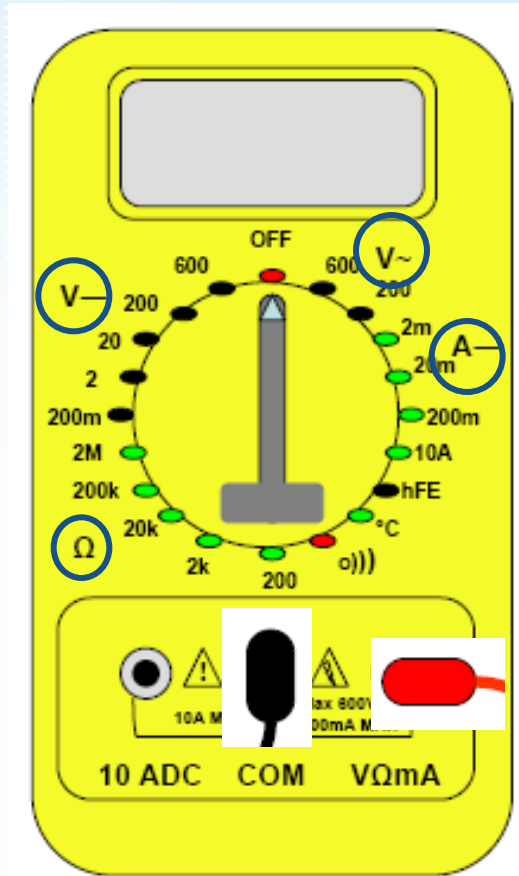Using a Voltmeter: connect probes (“test leads”)



for most measurements

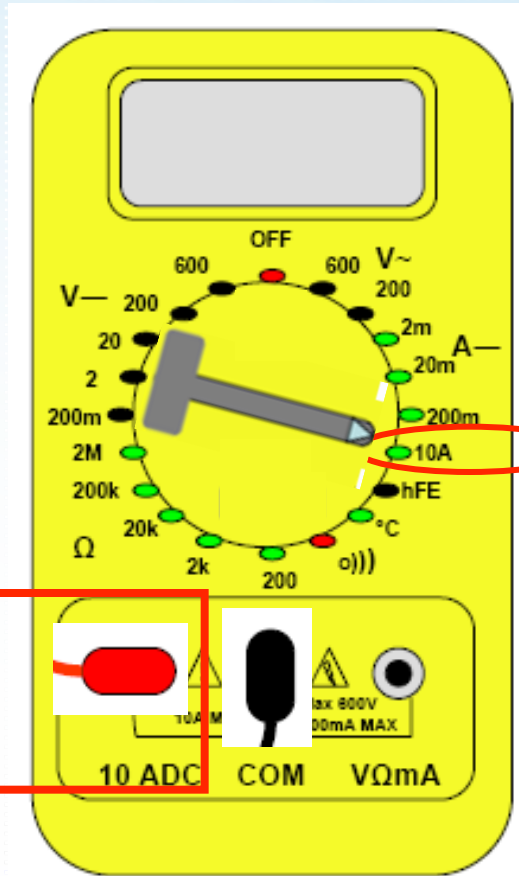
Using a Voltmeter: connect probes (“test leads”)



for high DC current
only


Do not leave
probe connected
like this!!!

Measuring Battery Voltage

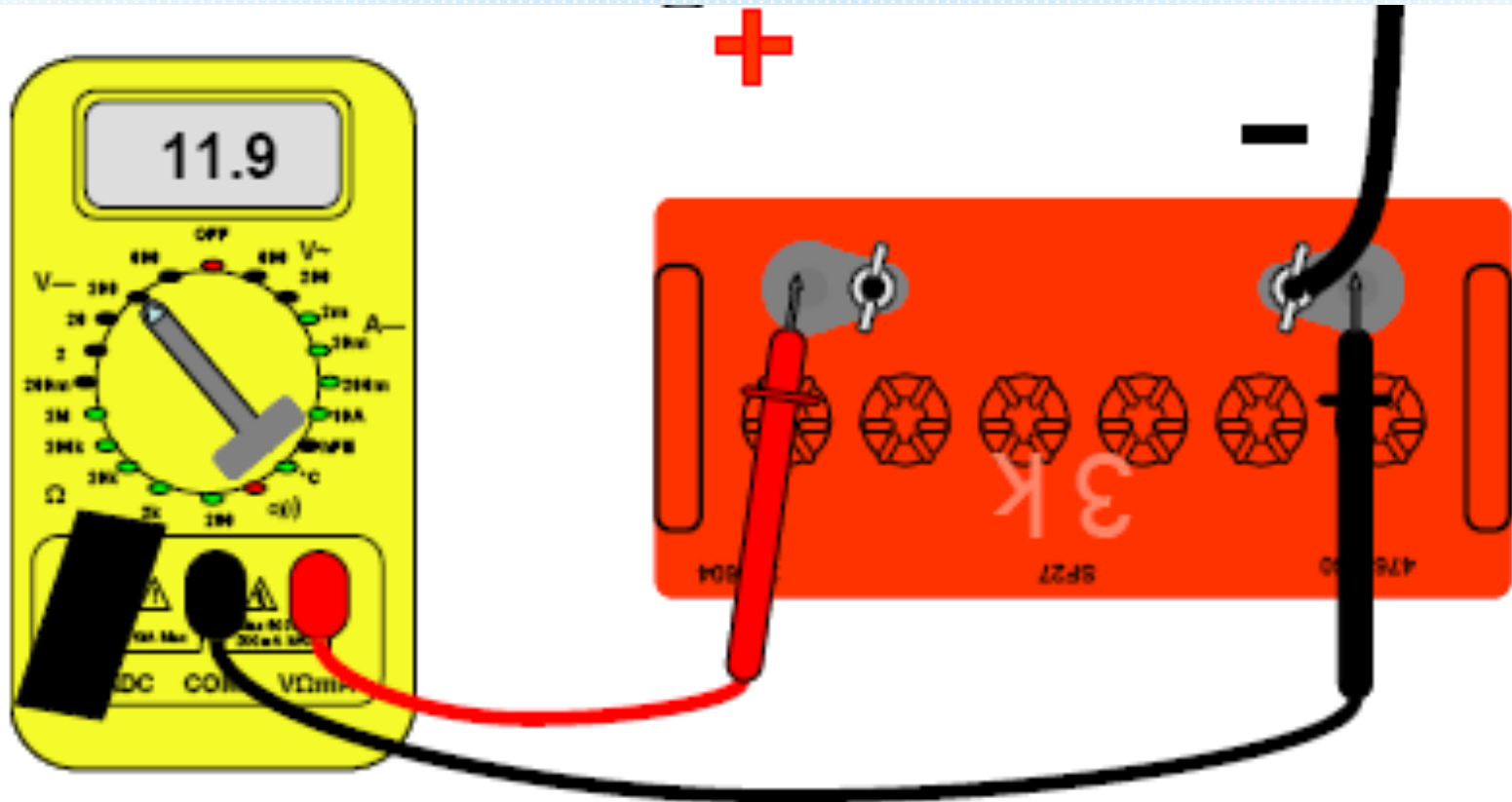

Warning!
DO NOT try to measure a (short circuit) battery current like this,
you would destroy the voltmeter!



Checking continuity

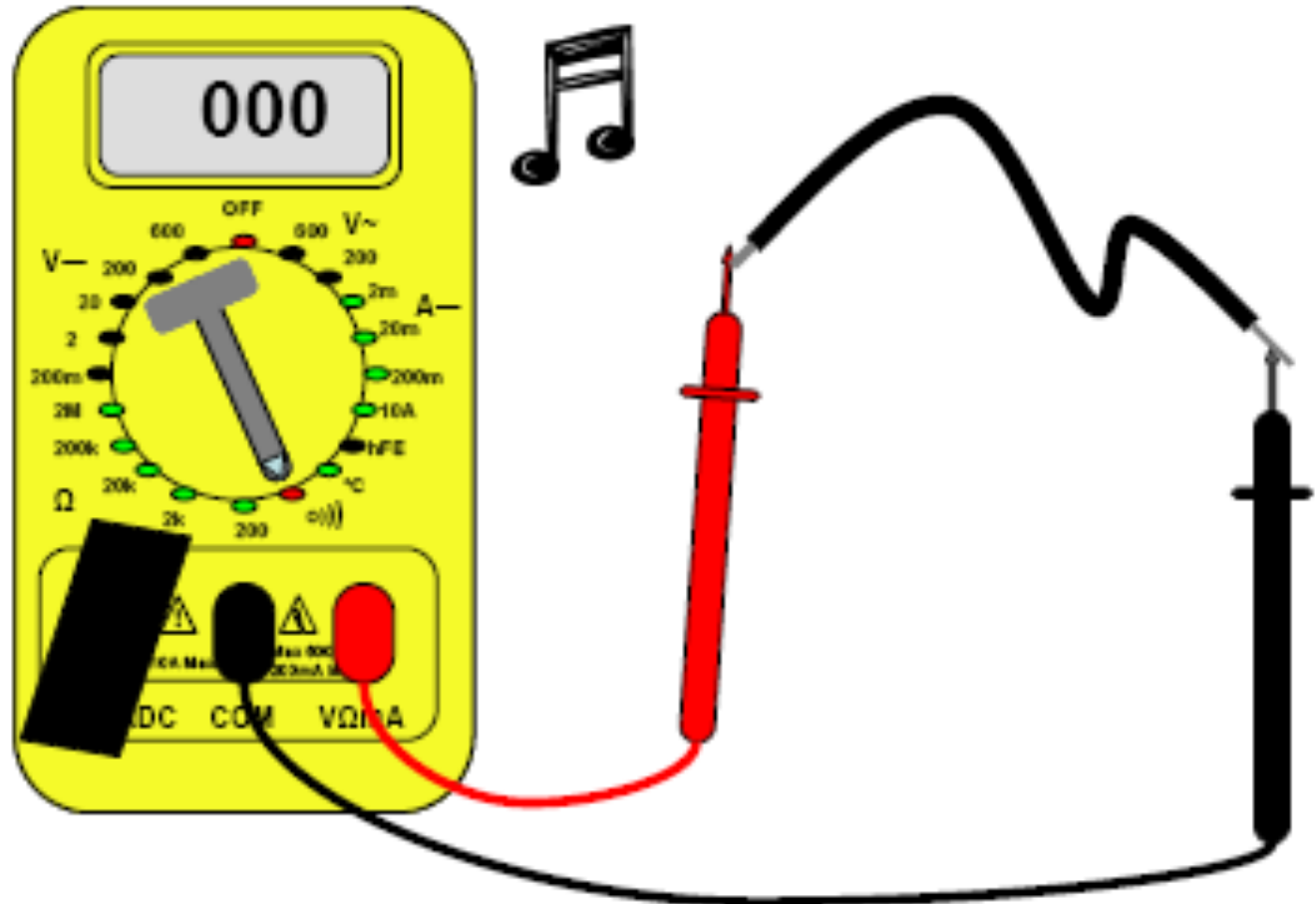

Basic Electricity – Demo

Using a basic circuit of light bulb socket + switch

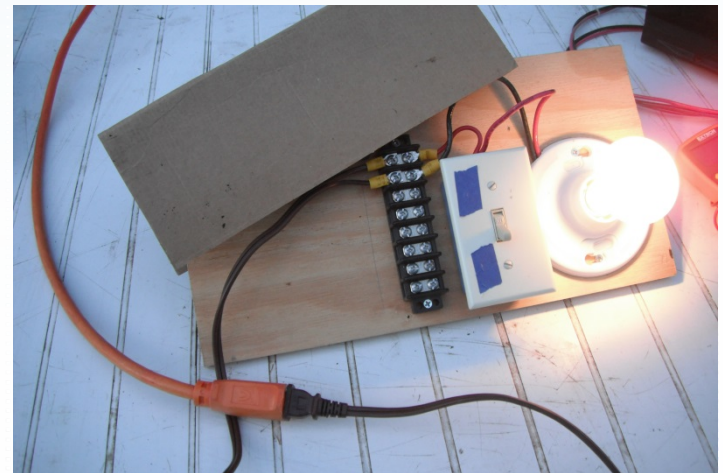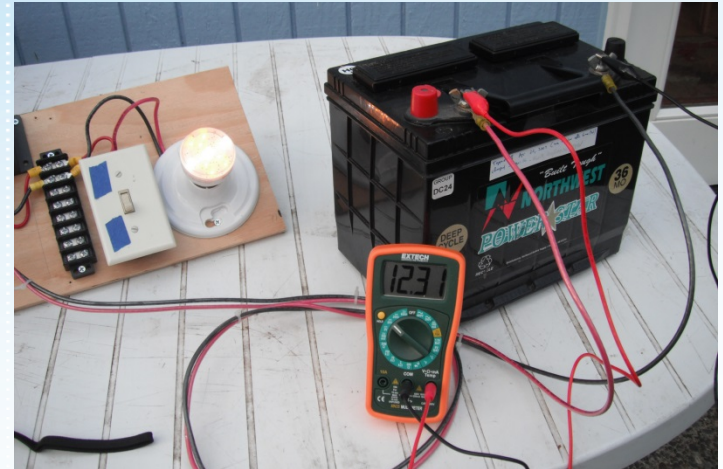- Install a 12V bulb, Connect to a 12V battery, measure voltage & current, compute power
- Install a 220V bulb, connect to AC outlet, measure voltage & current, compute power



Summary – Key Points

- Current symbol: '**I**', unit: '**A**' (Ampere or Amp)
 - $I = V / R$
- Voltage symbol: '**V**', Unit: '**V**' (Volt)
 - $V = I \times R$
- Resistance symbol: '**R**' and Unit: '**Ω**' (Ohm)
 - $R = V / I$
- Power symbol: '**P**' and Unit: '**W**' (Watt)
 - $P = I \times V$
- Meters
 - Multimeter and clamp meter
- AC: variable polarity and DC: fixed polarity